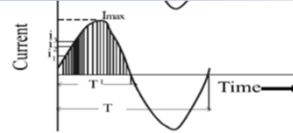


AC Circuits Basics of Electrical Engineering

BT © 2013

RMS Value (Root Mean Square Value)



$$\text{heat energy produced during 1st interval} = i_1^2 R \frac{T}{n} \text{ joule}$$

$$\text{heat energy produced during 2nd interval} = i_2^2 R \frac{T}{n} \text{ joule}$$

$$\text{heat energy produced during the nth interval} = i_n^2 R \frac{T}{n} \text{ joule}$$

$$\text{Total heat energy produced in the all n intervals} \quad W = RT \frac{(i_1^2 + i_2^2 + \dots + i_n^2)}{n}$$

$$W = I^2 RT \text{ joule}$$

BT © 2013

RMS Value (Root Mean Square Value)

$$I^2 RT = RT \frac{i_1^2 + i_2^2 + \dots + i_n^2}{n}$$

$$I^2 = \frac{i_1^2 + i_2^2 + \dots + i_n^2}{n} = \text{mean of square of instantaneous currents}$$


$$I = \sqrt{\frac{i_1^2 + i_2^2 + \dots + i_n^2}{n}} = \text{square root of mean of squares of instantaneous currents}$$

= Root mean square (RMS) value of current

$$E = \sqrt{\frac{e_1^2 + e_2^2 + \dots + e_n^2}{n}}$$

BT © 2013

RMS Value – Integral method

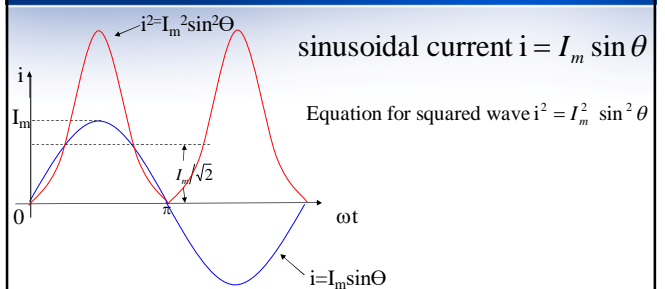

BT © 2013

RMS Value

The mean of the squares of instantaneous value of currents over the first half cycle
= area of the first half cycle of squared wave ÷ Its base

$$\begin{aligned} &= \frac{\int_0^\pi i^2 d\theta}{\pi} = \frac{1}{\pi} \int_0^\pi (I_m^2 \sin^2 \theta) d\theta \\ &= \frac{I_m^2}{\pi} \int_0^\pi \left(\frac{1 - \cos 2\theta}{2}\right) d\theta = \frac{I_m^2}{2\pi} \left[\theta - \frac{\sin 2\theta}{2}\right]_0^\pi \\ &= \frac{I_m^2}{2\pi} \times \pi = \frac{I_m^2}{2} \end{aligned}$$

root of mean of squares (rms value) $I = \sqrt{\frac{I_m^2}{2}} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$

BT © 2013

RMS Value

$$I_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2 d\theta}$$

$$E_{RMS} = \sqrt{\frac{1}{T} \int_0^T e^2 d\theta}$$

BT © 2013

Average Value

❖ Average value of an alternating quantity is defined as that steady direct current which transfers across any circuit the same amount of charge as is transferred by the alternating current during the same time

❖ 1) Mid ordinate method

$$I_{avg} = \frac{i_1 + i_2 + i_3 + \dots + i_n}{n}$$

BT © 2013

Average Value- Analytical Method


sinusoidal current $i = I_m \sin \theta$

$$I_{av} = \frac{\text{Area under half cycle}}{\pi}$$

$$= \frac{\int_0^\pi i d\theta}{\pi}$$

$$= \frac{1}{\pi} \int_0^\pi I_m \sin \theta d\theta$$
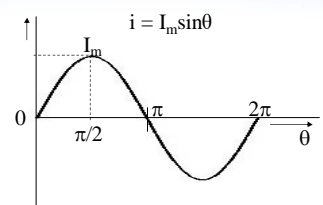
$$= \frac{I_m}{\pi} [-\cos \theta]_0^\pi = \frac{2I_m}{\pi}$$



$$I_{av} = 0.637 I_m$$

BT © 2013

Peak Factor/ Amplitude Factor (K_p)

$$\text{Peak factor} = \frac{\text{Maximum value}}{\text{RMS value}}$$

$$= \sqrt{2} \text{ for sinusoidal}$$

$$= 1.414$$

BT © 2013

Form Factor (K_f)

$$\text{Form Factor} = \frac{\text{RMS value}}{\text{Average value}}$$

$$= 1.11 \text{ for sinusoidal}$$


BT © 2013

Tutorial

Given $i = 62.35 \sin 323t$ A. Find f, I, I_m, I_{av}, K_f


BT © 2013

Phasor

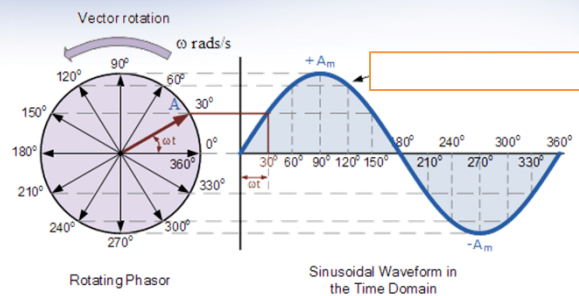


BT © 2013

In phase quantities

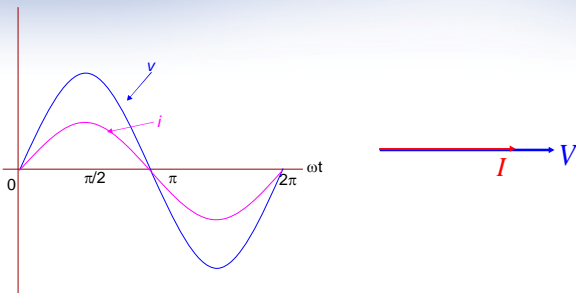


BT © 2013

Lagging current

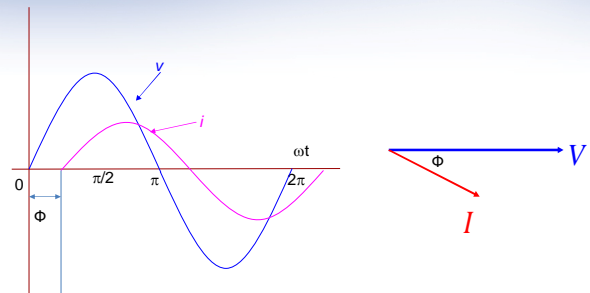

BT © 2013

Leading current

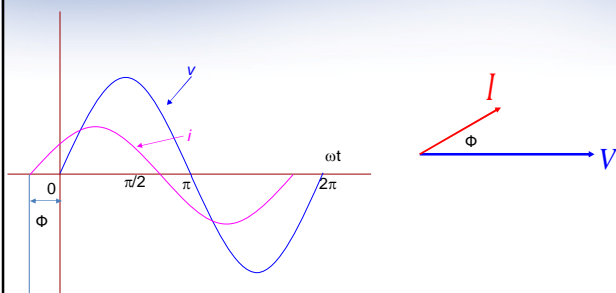

BT © 2013


- ❖ Phasors which reaches the vertical position first in the assumed direction of rotation is called leading

BT © 2013

AC Through a Purely Resistive Circuit

Let $v = V_m \sin \omega t$ ----- (1)

$$i = \frac{v}{R}$$

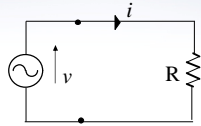

BT © 2013

AC Through a Purely Resistive Circuit

$$i = \frac{V_m}{R} \sin \omega t$$

i is maximum when $\sin \omega t$ is unity
ie

$$i = I_m \sin \omega t$$

$$I_m = \frac{V_m}{R}$$

$$I_{rms} = \frac{V_{rms}}{R}$$


$$V = IR$$

BT © 2013

AC Through a Purely Resistive Circuit

$$v = V_m \sin \omega t$$
 ----- (1)

$$i = I_m \sin \omega t$$
 ----- (2)

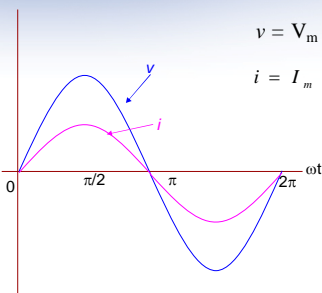

BT © 2013

Power in Purely R Circuit

$$p = vi$$

$$p = vi = V_m \sin \omega t \times I_m \sin \omega t$$

$$p = V_m I_m \sin^2 \omega t$$

$$p = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

$$p = \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t$$

Power consists of

□ Constant part $\frac{V_m I_m}{2}$

□ fluctuating part $\frac{V_m I_m}{2} \cos 2\omega t$

BT © 2013

Power in Purely R Circuit

❖ For complete cycle, average value $\frac{V_m I_m}{2} \cos 2\omega t$ is zero

❖ Power for whole cycle


$$= \frac{V_m I_m}{2}$$

$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}}$$

$$= V_{rms} I_{rms}$$

$$= VI = \frac{V^2}{R} = I^2 R$$

BT © 2013

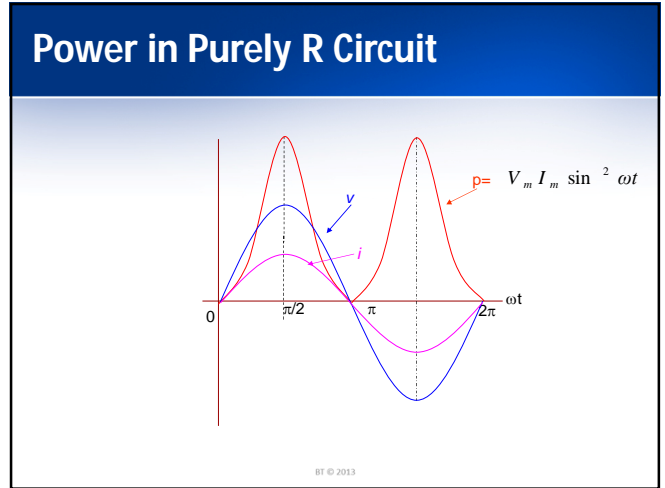

AC Through Purely Inductive Circuit

$v = V_m \sin \omega t$

Due to the inductance of the coil, a self induced emf $-L \frac{di}{dt}$ is induced in the coil which opposes the applied voltage at every instant

BT © 2013

AC Through Purely Inductive Circuit

$v = V_m \sin \omega t$ 1

where $I_m = \frac{V_m}{\omega L}$

$v = L \frac{di}{dt}$

From equ (1) and (2) it is clear that

$V_m \sin \omega t = L \frac{di}{dt}$

i lags behind v by $\frac{\pi}{2}$

$di = \frac{V_m}{L} \sin \omega t dt$

$i = \frac{V_m}{L} \int \sin \omega t dt$

$= \frac{V_m}{\omega L} (-\cos \omega t)$

$i = \frac{V_m}{\omega L} \sin (\omega t - \frac{\pi}{2})$

$i = I_m \sin (\omega t - \frac{\pi}{2})$2

BT © 2013

AC Through Purely Inductive Circuit

❖ Current through pure inductor lags the voltage across it by 90° .

$$V_m = \omega L I_m$$

$$= X_L I_m$$

$$X_L = \omega L = 2\pi f L \text{ ----- inductive reactance, in ohm}$$

$$I_m = \frac{V_m}{X_L} \quad \frac{I_m}{\sqrt{2}} = \frac{V_m/\sqrt{2}}{X_L} \quad \mathbf{I = \frac{V}{X_L}} \quad \mathbf{X_L = \frac{V}{I}}$$

BT © 2013


AC Through Purely Inductive Circuit

$$v = V_m \sin \omega t \text{1}$$

$$i = I_m \sin \left(\omega t - \frac{\pi}{2} \right) \text{.....2}$$

Phasor Diagram
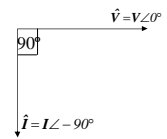
$$\frac{\bar{V}}{\bar{I}} = \frac{V \angle 0}{I \angle -90^\circ} = jX_L \text{ where } \frac{V}{I} = X_L$$



BT © 2013

Power in Purely L Circuit

$$p = vi$$

$$p = vi = V_m \sin \omega t \times I_m \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$p = -V_m I_m \sin \omega t \cos \omega t$$

Power for complete cycle


$$P = -\frac{V_m I_m}{2} \int_0^{2\pi} \sin 2\omega t$$

$$P = -\frac{V_m I_m}{2} \left[\frac{-\cos 2\omega t}{2} \right]_0^{2\pi} = 0$$

Average power demand is zero. However Maximum value of instantaneous power is $\frac{V_m I_m}{2}$

BT © 2013


Power in Purely L Circuit

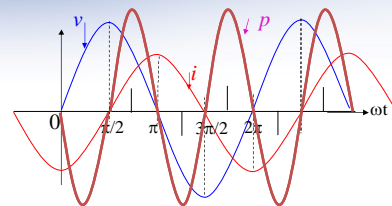

BT © 2013

AC Through Purely Capacitive Circuit

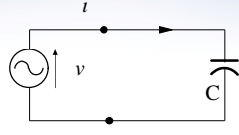- ❖ v- pd developed between the plates of capacitor at any instant
- ❖ q- Charge on plates at that instant
- ❖ q= Cv, where C is the capacitance



BT © 2013

AC Through Purely Capacitive Circuit

$$q = Cv$$

$$v = V_m \sin \omega t \dots (1)$$

$$q = CV_m \sin \omega t$$

$$i = \frac{dq}{dt}$$

$$i = \frac{d}{dt} (CV_m \sin \omega t)$$


$$i = \omega CV_m (\cos \omega t)$$

$$i = \frac{V_m}{1/\omega C} \sin(\omega t + \frac{\pi}{2})$$

$$i = I_m \sin(\omega t + \frac{\pi}{2}) \dots (2)$$

$$I_m = \frac{V_m}{1/\omega C} = \frac{V_m}{X_c}$$

$$X_c = \frac{1}{\omega C}$$

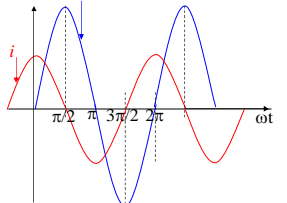


BT © 2013

AC Through Purely Capacitive Circuit

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$I_m = \frac{V_m}{X_c} \quad \frac{I_m}{\sqrt{2}} = \frac{V_m / \sqrt{2}}{X_c} \quad I = \frac{V}{X_c} \quad X_c = \frac{V}{I}$$

❖ Comparing equations (1) and (2) it is clear that i is leading v by 90°
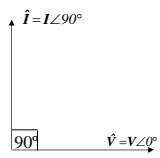
$$\frac{\bar{V}}{\bar{I}} = \frac{V \angle 0}{I \angle 90^\circ} = -jX_c \quad \text{where } \frac{V}{I} = X_c$$


BT © 2013

Power in Purely C Circuit

$$p = vi$$

$$p = v i = V_m \sin \omega t \times I_m \sin(\omega t + \frac{\pi}{2})$$

$$p = V_m I_m \sin \omega t \cos \omega t$$


Power for complete cycle

$$P = \frac{V_m I_m}{2} \int_0^{2\pi} \sin 2\omega t$$

$$p = \frac{V_m I_m}{2} \left[\frac{-\cos 2\omega t}{2} \right]_0^{2\pi} = 0$$

Average power demand is zero. However Maximum value of instantaneous power is $\frac{V_m I_m}{2}$

BT © 2013

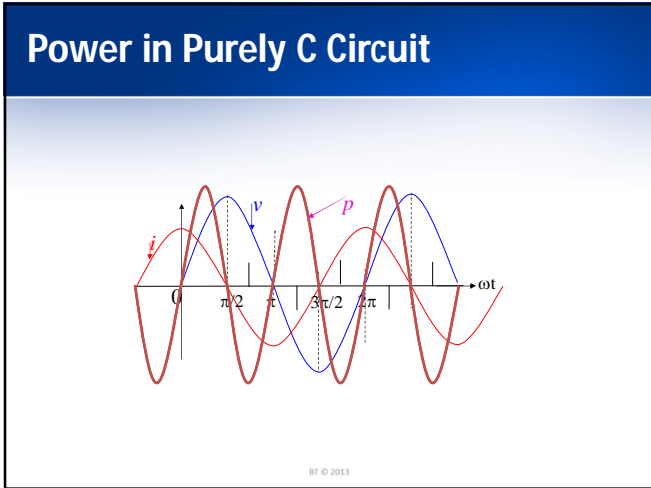

AC through Series RL Circuit

- ❖ V
- ❖ I
- ❖ $V_R = IR$
- ❖ $V_L = IX_L$

BT © 2013

AC through Series RL Circuit

$$V = \sqrt{V_R^2 + V_L^2}$$

$$V = \sqrt{(IR)^2 + (IX_L)^2}$$

$$V = I\sqrt{(R)^2 + (X_L)^2}$$

$$V = IZ$$

$$Z = \sqrt{(R)^2 + (X_L)^2}$$

$$\tan \phi = \frac{X_L}{R} = \frac{\omega L}{R} = \frac{\text{Reactance}}{\text{Resistance}}$$

Voltage Triangle

Impedance Triangle

BT © 2013

AC through Series RL Circuit

$v = V_m \sin \omega t$
 $i = I_m \sin(\omega t - \phi)$

BT © 2013

AC through Series RL Circuit

❖ Instantaneous power consumed $p = vi$

$$p = V_m \sin \omega t I_m \sin(\omega t - \phi)$$

$$p = V_m I_m \sin \omega t \sin(\omega t - \phi)$$

$$p = \frac{V_m I_m}{2} [\cos(\omega t - \omega t + \phi) - \cos(2\omega t - \phi)]$$

$$p = \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t - \phi)]$$

Constant part $\frac{V_m I_m}{2} \cos \phi$

Double frequency component $\frac{V_m I_m}{2} [\cos(2\omega t - \phi)]$

BT © 2013

AC through Series RL Circuit

Average Power = $\frac{V_m I_m}{2} \cos \phi$

Power = $VI \cos \phi$ $\cos \phi = \text{Power Factor}$

$$\cos \phi = \frac{R}{Z}$$

BT © 2013

BT © 2013

Power

- ❖ Apparent Power
 - ☐ Symbol- S
 - ☐ $S=VI$
 - ☐ Unit- VA (Volt Ampere) or kVA
- ❖ Active Power
 - ☐ Symbol - P
 - ☐ $P=VI \cos\phi$
 - ☐ Unit- W or kW
 - ☐ Power dissipated in resistive circuit
- ❖ Reactive Power
 - ☐ Symbol - Q
 - ☐ $Q=VI \sin\phi$
 - ☐ Unit - VAR (Volt Ampere Reactive) or kVAR

BT © 2013

Power in AC Circuit

Let Voltage be the reference $\bar{V} = V\angle 0$
 $\hat{Z} = Z\angle\phi \Rightarrow$ inductive load; then $\bar{I} = I\angle -\phi$

$$= I^2 Z\angle\phi = IZ(I \cos\phi + jI \sin\phi)$$

$$= VI(\cos\phi + j \sin\phi) = P + jQ$$

where $P = VI \cos\phi$, $Q = VI \sin\phi$

$$S = P + jQ$$

BT © 2013

Power Triangle

BT © 2013

AC through a series RC Circuit

- ❖ V
- ❖ V
- ❖ I
- ❖ $V_R = IR$
- ❖ $V_C = IX_C$

$$\bar{V} = \frac{V\angle 0}{I\angle 90^\circ} = -jX_C$$

BT © 2013

AC through a series RC Circuit

$$\bar{V} = \bar{V}_R + \bar{V}_C$$

$$V = \sqrt{V_R^2 + V_C^2}$$

$$V = \sqrt{(IR)^2 + (IX_C)^2}$$

$$V = I\sqrt{(R)^2 + (X_C)^2}$$

$$V = IZ$$

$$Z = \sqrt{(R)^2 + (X_C)^2}$$

$$\bar{V}_R = \bar{I}R + j0$$

$$\bar{V}_C = 0 - jI\bar{X}_C$$

BT © 2013

AC through a series RC Circuit


$$\hat{Z} = (R - jX_C) = Z \angle -\phi$$

$$= Z(\cos \phi - j \sin \phi)$$

$$R = Z \cos \phi; X_C = Z \sin \phi$$

$$\text{or } Z = \sqrt{(R^2 + X_C^2)};$$
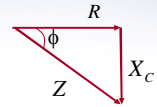
$$\phi = \tan^{-1}\left(\frac{X_C}{R}\right) = \tan^{-1}\left(\frac{1}{\omega CR}\right)$$




BT © 2013

AC through a series RC Circuit

$$i = I_m \sin \omega t$$

$$v = V_m \sin(\omega t - \phi)$$

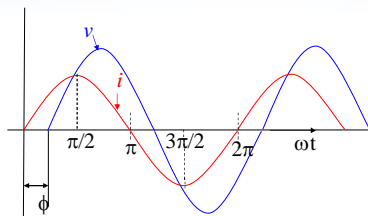

■ The current Leads behind the voltage by a phase angle ϕ

BT © 2013

Power in series RC and RL Circuit

❖ Derive it

BT © 2013

❖ Write down the frequency, rms and peak values of a voltage wave expressed as $v=14.1\sin 1000\pi t$. Write down the expressions for current flowing when this voltage is applied across a) 5Ω resistor, b) 1mH inductor and c) $150\mu\text{F}$ capacitor

BT © 2013

❖ A coil has an inductance of 20mH and a resistance of 5Ω . It is connected across a supply voltage of $v=50\sin 314t$. Obtain similar expression for current

BT © 2013

❖ In a given RL circuit, $R=3.5\Omega$ and $L=0.1\text{H}$. Find a) current through the circuit b) pf of a 50Hz voltage $V=220\angle 30^\circ$ is applied across it

BT © 2013

❖ An ac voltage $(80+j60)$ volts is applied to a circuit and current flowing is $(-4+j10)$ amperes. Find 1) impedance of the circuit and 2) power consumed and phase angle

BT © 2013

❖ A current of 5A flows through a non inductive resistance in series with a coil when supplied at 250V, 50Hz. If the voltage across the resistance is 125V and across the coil 200V. Calculate 1) impedance, resistance, and reactance of coil 2) power absorbed by the coil 3) total power. Draw Phasor diagram

BT © 2013

AC through Series RLC Circuit

V_L and V_C are out of phase by 180°

BT © 2013

AC through Series RLC Circuit

$$V = \sqrt{V_r^2 + (V_L - V_C)^2}$$

$$V = \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

$$V = I\sqrt{(R)^2 + (X_L - X_C)^2}$$

$$V = IZ$$

$$Z = \sqrt{(R)^2 + (X_L - X_C)^2}$$

BT © 2013

AC through Series RLC Circuit

❖ Let $i(t) = I_m \sin \omega t$

❖ Impedance, $Z = R + j(X_L - X_C)$

❖ (i) If $X_L = X_C$, resistive circuit

❖ (ii) If $X_L > X_C$, RL series circuit

❖ (iii) If $X_L < X_C$, RC series circuit

Note: $-i(t)$ is the reference

Circuit Elements	Impedance Z	Phase Angle ϕ
	R	0°
	X_C	-90°
	X_L	$+90^\circ$
	$\sqrt{R^2 + X_C^2}$	Negative, between -90° and 0°
	$\sqrt{R^2 + X_L^2}$	Positive, between 0° and 90°
	$\sqrt{R^2 + (X_L - X_C)^2}$	Negative if $X_C > X_L$ Positive if $X_C < X_L$

Parallel RLC Circuit

$v = V_m \sin \omega t$
 $\vec{V} = V \angle 0$

Phasor Diagram -

$\vec{I}_R = \frac{V}{R} \angle 0$; $\vec{I}_L = \frac{V}{X_L} \angle -90$;
 $\vec{I}_C = \frac{V}{X_C} \angle 90$

BT © 2013

Parallel RLC Circuit

For any parallel circuit,
 $Y = \frac{1}{Z} = \text{Admittance}$
 $= G \pm jB$

Unit is Siemens
 Where G = Conductance
 B = Susceptance

BT © 2013

Parallel RLC Circuit

For any parallel circuit

$Y_1 = \frac{1}{Z_1}; Y_2 = \frac{1}{Z_2}; \dots; Y_N = \frac{1}{Z_N}$
 $Y_{eq} = Y_1 + Y_2 + \dots + Y_N = \frac{1}{Z_{eq}} = G_{eq} \pm jB_{eq}$
 $I_1 = VY_1; I_2 = VY_2; \dots; I_N = VY_N$
 $I = I_1 + I_2 + \dots + I_N = VY_{eq}$

ELE101/102 Dept of E&E, MIT Manipal 59

Problem

Two circuits $Z_A = 5 + j2 \Omega$ and $Z_B = 6 - j8 \Omega$ are in parallel across a 200V, 50 Hz supply. Find current in each branch, total current, power factor and power consumed.

Ans: $\vec{I}_A = 37.14 \angle -21.8^\circ \text{A}$ $\vec{I}_B = 20 \angle 53.13^\circ \text{A}$
 $I = 46.54 \angle 2.72^\circ \text{A}$ $\cos \phi = 0.9988 \text{ lead}$
 Power = 9.297W

BT © 2013